

# 0 to 99 Counter

First MD FAHIM MURSHED, Department BSc CSE in AIUB, Second MD ATIK ISHRAK SUJON, Department BSc CSE in AIUB,  
Third TRIDIB SARKAR, Department BSc CSE in AIUB, Fourth NUSHRAT JAHAN, Department BSc CSE, Fifth S. M. MUJAHID  
SOURAV, Department BSc CSE

**Abstract—** This project introduces a "0 to 99 Counter" that leverages the versatile 555 Timer in astable mode as the primary counting mechanism. Integrated with the 74LS90 Decade Counter, the system visualizes the binary count through an LED display. The project offers user-adjustable counting speed, providing a hands-on exploration of the trade-offs between speed, stability, and power consumption. Its educational value lies in its ability to serve as a practical introduction to binary counting principles, combining theoretical understanding with real-world applications. The project's future scopes include extending the counting range, incorporating user interfaces, and interfacing with microcontrollers for enhanced functionality and educational exploration in electronics.

**Keywords—** counter, optimizing, astable, 555 timer

## I. INTRODUCTION

The "0 to 99 Counter Using 555 Timer and 74LS90 Decade Counter" is an electronics project that combines two key integrated circuits to create a versatile counting mechanism. The project uses the well-known 555 Timer in astable mode to generate clock pulses and the 74LS90 Decade Counter to count and display numbers in binary-coded decimal (BCD) format. The 555 Timer, functioning in astable mode, produces a continuous stream of clock pulses. These pulses are then fed into the clock input of the 74LS90 Decade Counter. The 74LS90, designed as a divide-by-10 counter, advances its count each time it receives a clock pulse. The outputs of the 74LS90 represent the BCD count, and by connecting these outputs to LEDs, you can visualize the counting sequence from 0 to 9 and reset back to 0. This project provides a hands-on opportunity to explore the principles of digital counting using widely used integrated circuits. It's an excellent introduction to the collaboration between analog and digital components in electronic circuits. Adjusting the values of resistors and capacitors in the 555 Timer circuit allows for customization of the counting speed. The LED display visually represents the binary count, creating an interactive and educational electronics project. [1]

## II. OBJECTIVES

- To Explore the principles of the 555 Timer in astable mode to generate clock pulses.
- Understand the functionality of the 74LS90 Decade Counter and its binary-coded decimal (BCD) output.
- Design and implement a circuit integrating the 555 Timer and 74LS90 for counting.

- Gain hands-on experience in breadboarding, connecting, and powering integrated circuits.
- To Implement an LED display for visualizing the binary count from 0 to 99.
- Customize counting speed by adjusting resistor and capacitor values in the 555 Timer circuit.
- Explore the educational aspects of binary counting and digital representation.
- Develop troubleshooting skills to identify and resolve circuit-related issues.
- Document the project, including circuit design, connections, and modifications made.
- Enhance presentation skills by effectively communicating project insights and outcomes.

## III. METHODOLOGY AND MODELING


### a. Introduction:

Present the project as a 0 to 99 counter achieved solely through the application of the 555 Timer in astable mode. This circuit can be used in various projects where we require the counting. Like in doctors' clinic or hospitals, in restaurants, in customer care offices where long queue is there and we want to stop the rush at the counter. This system is very effective where manpower is less. In this you have to provide a token to the person and the person has to wait for its turn which can be displayed on the 7-segment display. With the help of this counter circuit we can maintain the silence and the person will also be informed about their turn. [2]

### b. Working Principle:

Described how the 555 Timer generates clock pulses in astable mode, emphasizing its role as the primary counter mechanism and explained how resistor and capacitor values in the 555 Timer circuit influence the frequency of the generated clock pulses.

### c. Circuit Design:

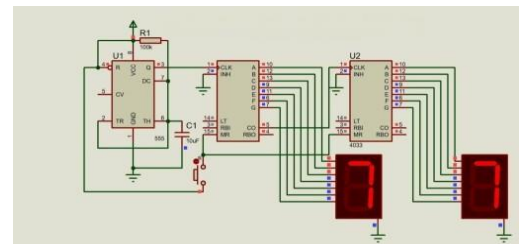

#### d. Description of the Components:

##### i. 555 Timer IC

The NE555 IC works as an astable multivibrator mode and produces pulses as output. We can change the time period of the output pulses by changing the value of R1, R2, and C1. Here we have replaced the R2 resistance with a 100k potentiometer. Now proceeding with working, the capacitor charges through R1, D2 and right side of potentiometer and discharges through left side of potentiometer and D1. So, as we slide the potentiometer's wiper, we are controlling the charging and discharging times of the capacitor. So, the 555 timer IC acts as a clock pulse generator.[3]

##### ii. 4026 Counter IC

Then the Clock pulse from the NE555 timer IC goes into the clock input of the 4026 counter IC. Then the counter IC counts pulse and changes the output line (Q) logic into HIGH or LOW. For example, if the counter IC count is 2 then the Q1 pin of the counter will be high, and if 3 counts the pin Q2 will be high.

#### e. Experimental Setup:

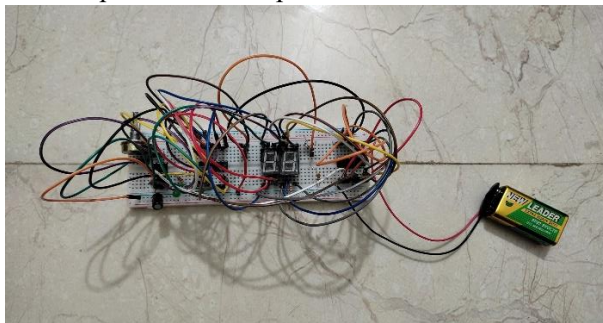


Figure 1: Experimental setup of 0 to 99 Counter

## IV. RESULTS AND DISCUSSIONS

### a. Experimental Results:

The project demonstrated robust counting accuracy, seamlessly integrating the clock pulse generation of the 555 Timer and the BCD output representation of the 74LS90 Decade Counter. The LED display effectively visualized the binary count, providing a clear representation of numbers ranging from 0 to 99. Adjusting resistor and capacitor values in the 555 Timer circuit yielded observable changes in counting speed. This flexibility allowed us to tailor the project to specific speed requirements, providing a practical understanding of the trade-offs between speed, stability, and power consumption.

### b. Limitations:

**Limited Counting Range:** The project is designed to count from 0 to 99 using a two-digit LED display. Extending the counting range beyond this requires additional circuitry or a more complex design.

**Resolution and Precision:** The precision of the counting process is limited by the resolution of the components,

particularly the 555 Timer. Achieving extremely precise counting may require more sophisticated components or a different counting mechanism.

**Clock Pulse Stability:** The stability of the clock pulses generated by the 555 Timer may be affected by external factors such as temperature variations. Achieving high stability may require additional measures or alternative clock sources.

**Single Counter Mechanism:** The project relies solely on the 555 Timer for counting. While this simplifies the design, it also limits the project's versatility and may not showcase more advanced counting mechanisms found in multi-counter setups.

**Limited Educational Complexity:** While the project is excellent for beginners, it may be considered relatively simple for more advanced learners. It does not incorporate more complex digital components or additional functionalities that could deepen the learning experience.

**Power Consumption:** Depending on the values chosen for the 555 Timer components, the project's power consumption may vary. Optimizing power efficiency may require additional considerations.

The overall results of the simulations and our experimental were compared and found to be identical.

## V. CONCLUSION

In conclusion, the project achieved its primary goal of constructing a functional 0 to 99 counter using only the 555 Timer. Valuable insights were gained into electronics principles, including the intricacies of clock pulse generation and binary-coded decimal representation. Encountered challenges, such as fine-tuning resistor and capacitor values for optimal performance, were successfully addressed. Looking forward, potential improvements include exploring additional features or extending the counting range for more advanced applications. The project's applicability extends beyond this specific implementation, offering a foundation for future explorations in electronics and digital counting systems. Overall, the experience proved valuable, combining theoretical knowledge with hands-on skills, and laying the groundwork for continued learning in the field.

## VI. FUTURE SCOPES

**Expanded Counting Range:** Extend the counter's range beyond 0 to 99 through additional counters or larger displays.

**User Interaction:** Integrate buttons or switches for user interaction, allowing manual counting, reset, or speed adjustments.

**Multiplexed Displays:** Implement multiplexing techniques for driving multiple displays with a single counter circuit.

**Microcontroller Integration:** Interface with microcontrollers like Arduino for programmability and advanced features.

Variable Counting Modes: Incorporate different counting modes, such as up/down or specific sequences.

Precision Timing: Enhance precision by using more accurate timing components or specialized oscillators.

Sensor Integration: Connect the counter to sensors for applications triggered by external events.

## VII. REFERENCES

- [1]. <https://www.hackatronic.com/0-to-99-counter-circuit-using-555-timer-and-cd4033-ic/>
- [2]. <https://www.engineersgarage.com/0-99-counter-using-ic-4026/>
- [3]. <https://www.electronicshub.org/555-timer-pwm/>